
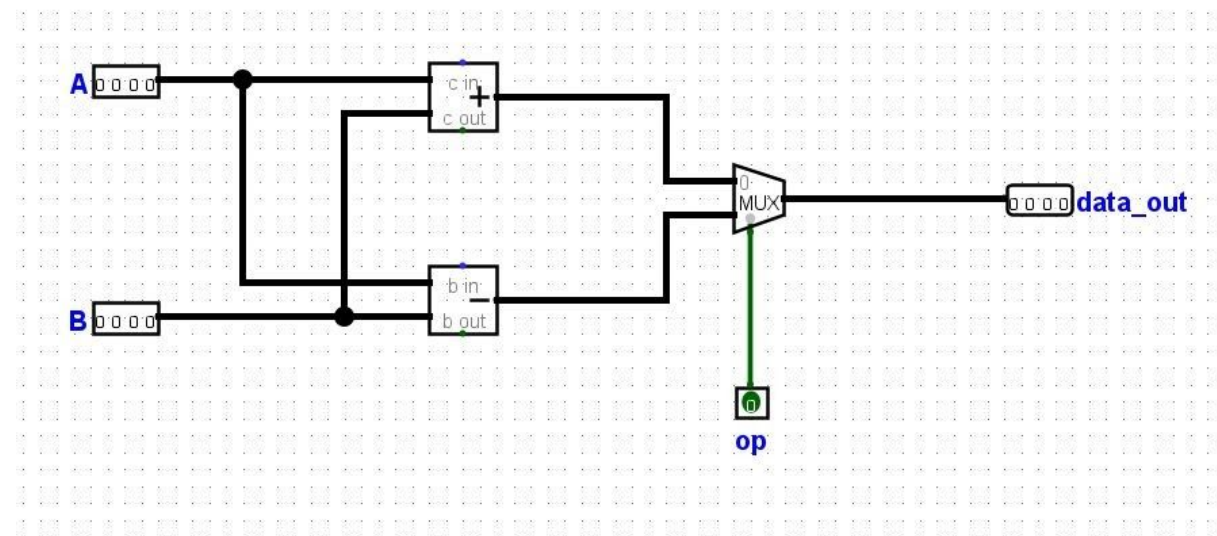


CSC258 lab7  
Haodong Mai  
1004321646  
PRA0105


## ALU

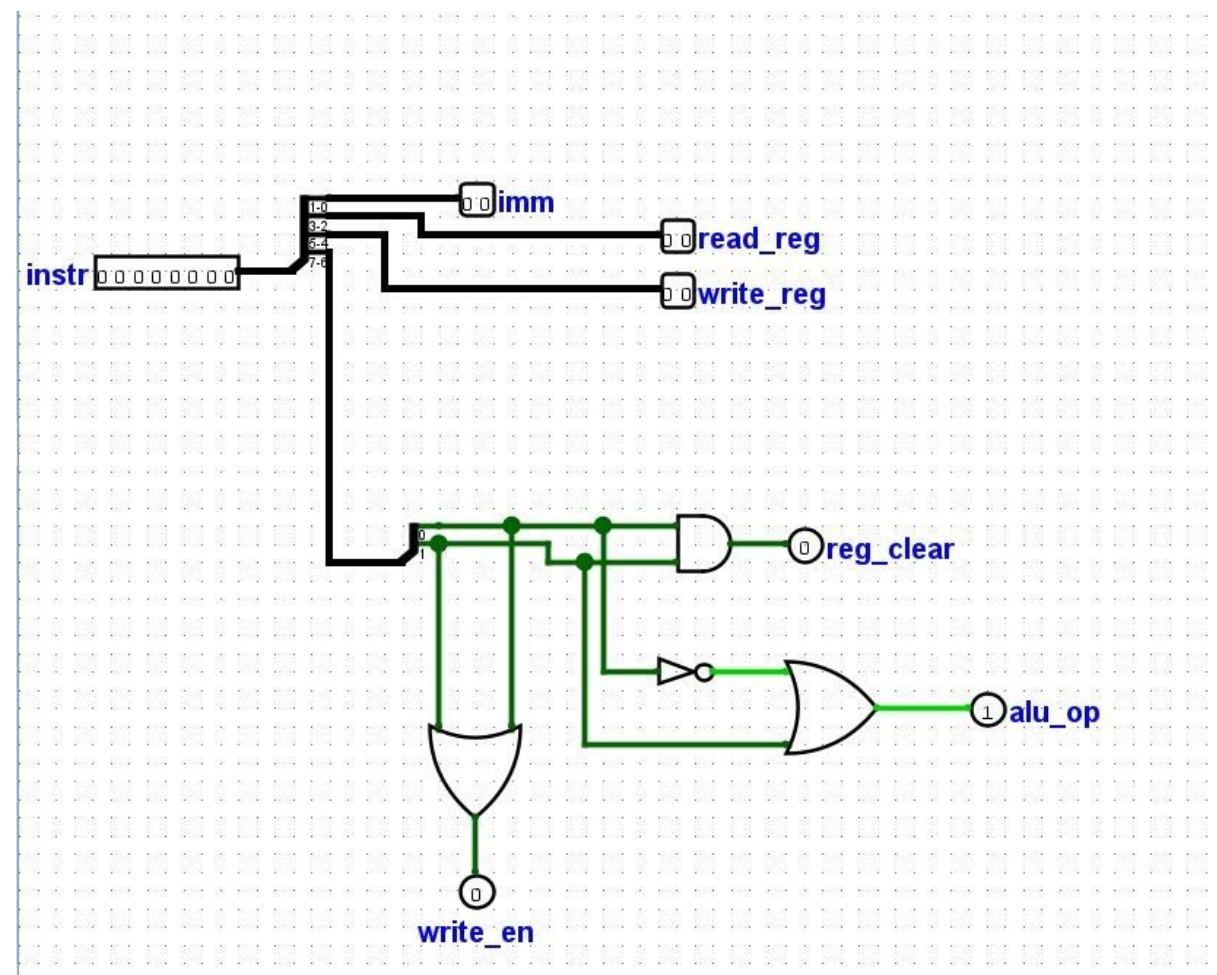

instruction decoder



main

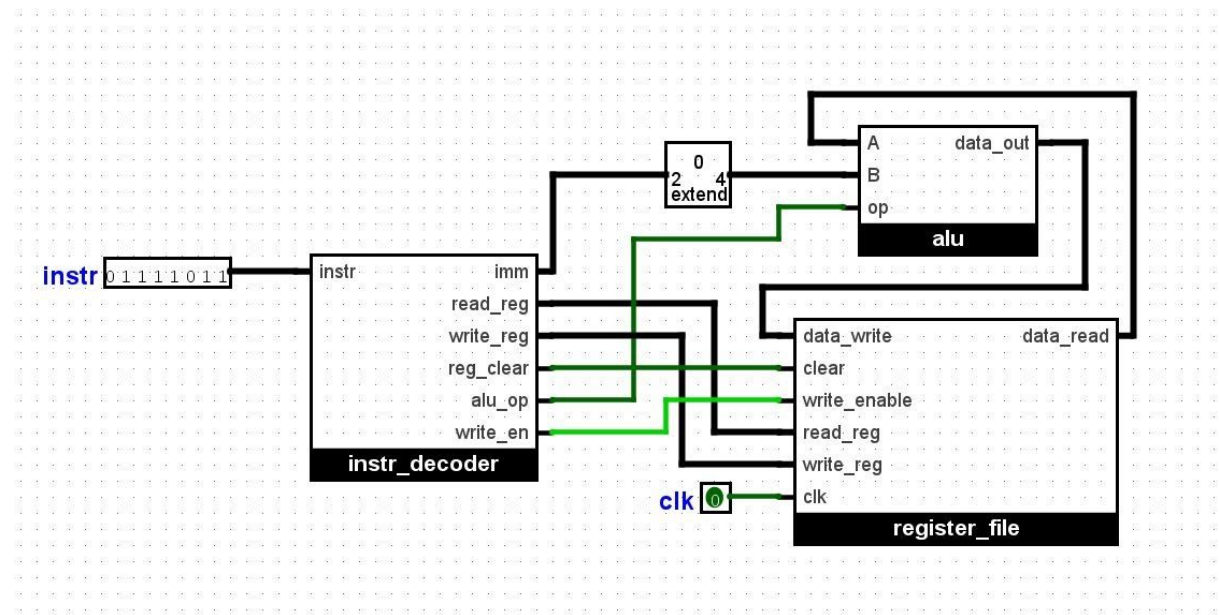

Example machine instruction: 01100011

Start with the following state(before execution): reg0=4;reg1=3;reg2=0;reg3=0

The machine instruction is decoded as follows:

imm=3;

Src reg= reg0;

Dest reg=reg2;

op= ALU operation A;

The whole instruction is src\_reg ALU operation A imm and write the result to dest\_reg.

The alu\_op is set to low to select the ALU operation A output(high for operation B).

The write\_en is set to high for writing the ALU output to dest\_reg.

The reg\_clear is set to low since the op code is not CLEAR DEST REG(ie.11).

In a clock cycle, the ALU takes the value from reg0 and performs addition with imm.

Then the selected ALU output(4+3=7) is sent to data\_write to be written to reg2.

Finally, we have the state: reg0=4;reg1=3;reg2=7;reg3=0.