

CSC258 lab3 Haodong Mai 1004321646 PRA0105


## Circuit diagram of mux6-to-1:

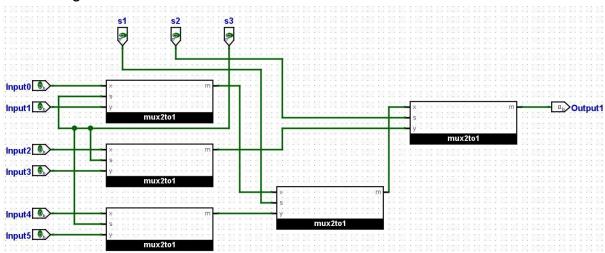

## Circuit diagram of demux1-to-6:

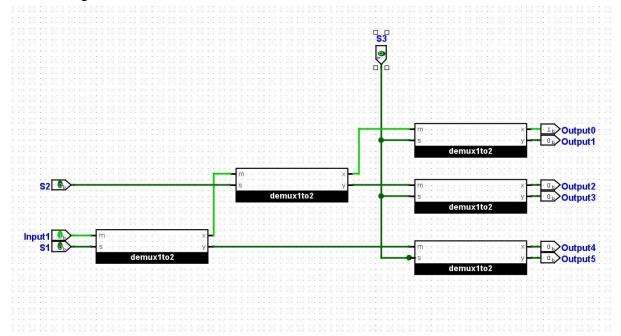
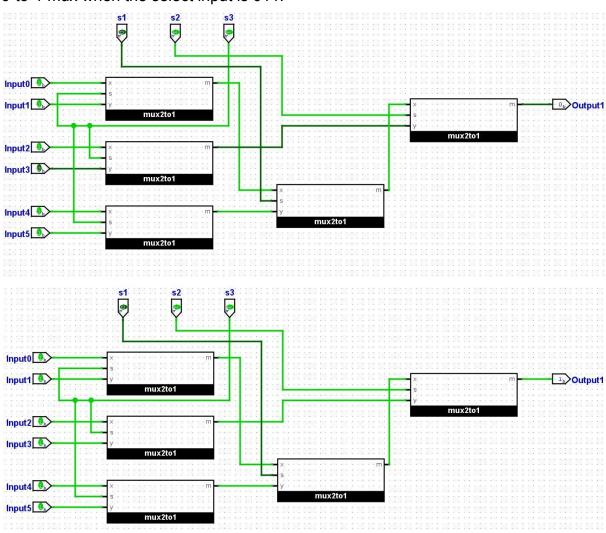
## 6-to-1 mux when the select input is 011:



## 1-to-6 demux when the select input is 101:

